

**Dan Otieno**

**EE 316 Lab 2: Pre-Lab Assignment.**

**Due date: 08/29/22.**

**Assignment details:**

Read Lab 2 manual and understand how inverting and non-inverting operational amplifier circuits work. Fill the "Theoretical Results" columns from Table 2.1 through 2.4.

**DC source:**

**$V_{in} = 1V$ ,  $R_{in} = 1K$**

**Table 2.1 (Inverting Amplifier)**

|           | Theoretical Results |      | Multisim Results |      | Lab Results   |      |
|-----------|---------------------|------|------------------|------|---------------|------|
| $R_F$ (K) | $V_{OUT}$ (V)       | Gain | $V_{OUT}$ (V)    | Gain | $V_{OUT}$ (V) | Gain |
| 0.5       | -0.5                | -0.5 | -0.498           |      |               |      |
| 1         | -1                  | -1   | -0.998           |      |               |      |
| 2         | -2                  | -2   | -1.997           |      |               |      |
| 3         | -3                  | -3   | -2.996           |      |               |      |
| 4         | -4                  | -4   | -3.994           |      |               |      |

**Table 2.2 (Non-Inverting Amplifier)**

|           | Theoretical Results |      | Multisim Results |      | Lab Results   |      |
|-----------|---------------------|------|------------------|------|---------------|------|
| $R_F$ (K) | $V_{OUT}$ (V)       | Gain | $V_{OUT}$ (V)    | Gain | $V_{OUT}$ (V) | Gain |
| 0.5       | 1.5                 | 1.5  |                  |      |               |      |
| 1         | 2                   | 2    |                  |      |               |      |
| 2         | 3                   | 3    |                  |      |               |      |
| 3         | 4                   | 4    |                  |      |               |      |
| 4         | 5                   | 5    |                  |      |               |      |

AC source:  
 $V_{in} = 2V_{pp}$ ,  $R_{in} = 1K$

**Table 2.3 (Inverting Amplifier)**

|           | Theoretical Results |      | Multisim Results |      | Lab Results   |      |
|-----------|---------------------|------|------------------|------|---------------|------|
| $R_F$ (K) | $V_{OUT}$ (V)       | Gain | $V_{OUT}$ (V)    | Gain | $V_{OUT}$ (V) | Gain |
| 0.5       | -1                  | -0.5 | 0.997            | 0.5  |               |      |
| 1         | -2                  | -1   | 2                | 1    |               |      |
| 2         | -4                  | -2   | 3.98             | 1.99 |               |      |
| 3         | -6                  | -3   | 5.99             | 2.99 |               |      |
| 4         | -8                  | -4   | 7.99             | 3.99 |               |      |

**Table 2.4 (Non-Inverting Amplifier)**

|           | Theoretical Results |      | Multisim Results |      | Lab Results   |      |
|-----------|---------------------|------|------------------|------|---------------|------|
| $R_F$ (K) | $V_{OUT}$ (V)       | Gain | $V_{OUT}$ (V)    | Gain | $V_{OUT}$ (V) | Gain |
| 0.5       | 1.5                 | 3    | 3                | 1.5  |               |      |
| 1         | 2                   | 4    | 3.98             | 1.99 |               |      |
| 2         | 3                   | 6    | 5.98             | 3    |               |      |
| 3         | 4                   | 8    | 7.99             | 4    |               |      |
| 4         | 5                   | 10   | 9.99             | 5    |               |      |