

Theoretical Analysis for figure 6.3.

Waveform for node A in two cycles is in red.

Waveform for mode c is in yellow.

Waveform for mode D is in purple.


PHASE RELATIONSHIPS.

- ① $\angle \theta_A - \angle \theta_C = 0^\circ$
- ② $\angle \theta_A - \angle \theta_D = -180^\circ$
- ③ $\angle \theta_C - \angle \theta_D = 0^\circ$

- From A to C, voltages are in phase.
- From C to D, voltages are 180° out of phase.

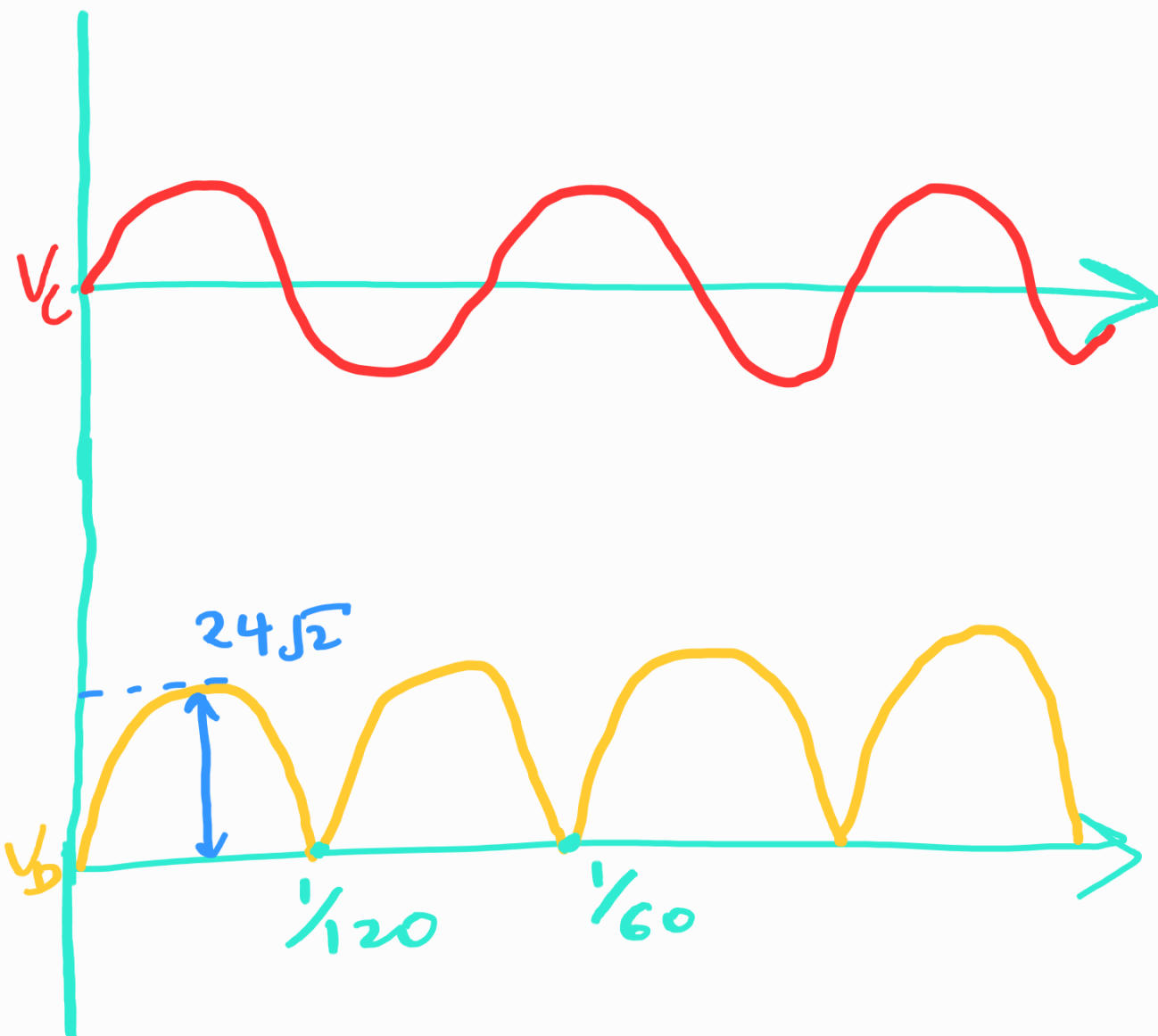PART 2:

- For figure 6.4, V_{out} for a few cycles:



- DC value of V_{out} :

$$V_{out} = \frac{2 \cdot 24\sqrt{2}}{\pi}$$

$$= \frac{67.882}{\pi}$$

$$= \boxed{21.6 \text{ V}}$$

- Ripple frequency:

$$= \frac{1}{120} = \boxed{120 \text{ Hz}}$$