

Dan Otieno

EE 316 Lab 3: Pre-Lab Assignment.

Due date: 09/11/22.

Assignment details:


Read Lab 3 manual and calculate output voltage for figure 3.2 given the following conditions:

$R = 1 \text{ ohm}$.

$C = 1 \text{ F}$.

$V_{in} = \sin(t)$.

Given the figure below:

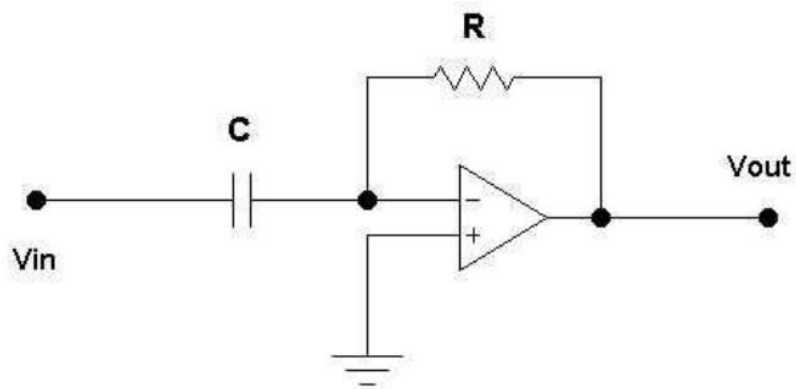

We know that:

$$V_{OUT}(t) = -RC \frac{dV_{IN}(t)}{dt}$$

Dan Otieno

$$R = 1 \Omega.$$

$$C = 1 F.$$

$$V_{in} = \sin(t).$$

$$V_{out}(t) = -(1)(1)(\sin(t)) \quad * \quad d/dt(\sin(t)) = \cos(t).$$

$$\therefore V_{out}(t) = \boxed{-\cos(t)}$$